

## MINI PROJECT-2

**TOPIC:** Design an Audio Amplifier circuit and measure the output power.

### **2.1 INTRODUCTION**

This project entails the creation of an audio amplifier circuit utilizing a UA741 operational amplifier along with CL100 and CK100 transistors to boost audio signals and measure the resultant output power. The objective is to grasp the functioning of audio amplifiers, their components, and their practical applications in everyday scenarios.

Audio amplifiers play a critical role in various electronic devices, such as radios, televisions, smartphones, and home theater systems, by enhancing the quality and strength of audio signals. An amplifier elevates a weak input signal to a higher level, making it appropriate for driving loudspeakers and other audio output devices.

The UA741 operational amplifier is a commonly used element in audio amplification due to its reliability and flexibility. It acts as the pre-amplifier stage, where the initial audio signal is amplified before being further boosted by the power amplifier stage, which in this project employs CL100 and CK100 transistors. These transistors are selected for their capability to handle higher power levels, making them ideal for driving the output load, which in this scenario, is a speaker.

This practical project not only reinforces the theoretical knowledge acquired during coursework but also provides essential insights into practical electronics, which is crucial for future projects and professional endeavors in the field of electronics and communication engineering.

### **2.2 LITERATURE SURVEY**

#### **Overview of Existing Works:**

Audio amplifiers are essential components in electronic systems, designed to enhance audio signals for improved sound quality and sufficient power to drive speakers. Various amplifier classes have been developed, each with unique characteristics and applications.

- **Class A Amplifiers:** Renowned for their excellent linearity and minimal signal distortion, Class A amplifiers operate with the active device (transistor or vacuum tube) conducting throughout the entire input signal cycle. While they deliver high-fidelity audio output, they also suffer from significant power dissipation and low efficiency, typically ranging from 20-30% [1].

- **Class B Amplifiers:** These amplifiers improve efficiency by having the active device conduct for only half of the input signal cycle. This design, however, introduces crossover distortion at the transition point between the positive and negative halves of the signal, potentially degrading audio quality [2].
- **Class AB Amplifiers:** Combining the benefits of Class A and Class B, Class AB amplifiers conduct for more than half but less than the entire signal cycle. This design reduces crossover distortion and improves efficiency to about 50-70% compared to Class A amplifiers [2].
- **Class D Amplifiers:** Achieving high efficiency (over 90%) through pulse-width modulation (PWM), Class D amplifiers convert the input signal into a series of high-frequency pulses. The complexity of the circuit design and potential electromagnetic interference (EMI) require careful filtering to maintain audio fidelity [3].

#### **Disadvantages of Existing Works:**


- **Class A Amplifiers:** Although they offer high-fidelity output, their continuous operation results in high power consumption and significant heat dissipation, making them less suitable for portable or energy-efficient applications [1].
- **Class B Amplifiers:** The main drawback is the introduction of crossover distortion at the zero-crossing point of the input signal, which can cause noticeable audio distortion at low signal levels [2].
- **Class AB Amplifiers:** While these amplifiers strike a balance between Class A and Class B, they still face challenges with heat dissipation and slightly higher power consumption compared to Class B designs [2].
- **Class D Amplifiers:** Despite their high efficiency, the complex circuitry and the need for effective EMI management make these amplifiers more challenging to design and implement. The switching nature of Class D amplifiers can also introduce high-frequency noise that must be filtered out to prevent audio distortion [3].

#### **Research Insights:**

Recent research has been directed towards enhancing the efficiency and performance of audio amplifiers. For instance, a study by Gupta et al. (2021) explores advanced techniques in Class D amplifier design to reduce EMI and improve audio quality through enhanced filtering methods [1]. Another paper by Johnson et al. (2020) investigates hybrid amplifier designs that combine elements of Class AB and Class D to balance efficiency and audio fidelity [2]. Additionally, the integration of

digital signal processing (DSP) in modern audio amplifiers has been recognized as a significant advancement, allowing for more precise control over audio output and the mitigation of distortion issues [3].

### 2.3 BLOCK DIAGRAM

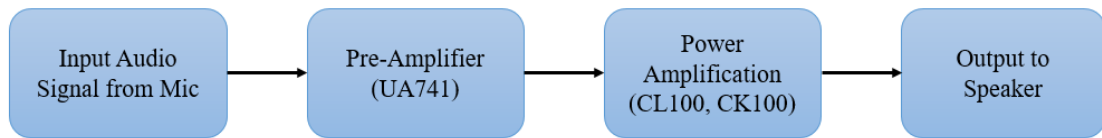


### 2.4 FLOWCHART/ALGORITHM


#### Algorithm:

1. **Input Stage:** Receive the input audio signal.
2. **Pre-Amplification:** Boost the audio signal using UA741 operational amplifier.
3. **Power Amplification:** Further amplify the signal using CL100 and CK100 transistors.
4. **Output Stage:** Deliver the amplified audio signal to the speaker.
5. **Measurement:** Measure the output power using appropriate instruments.

#### Flowchart:

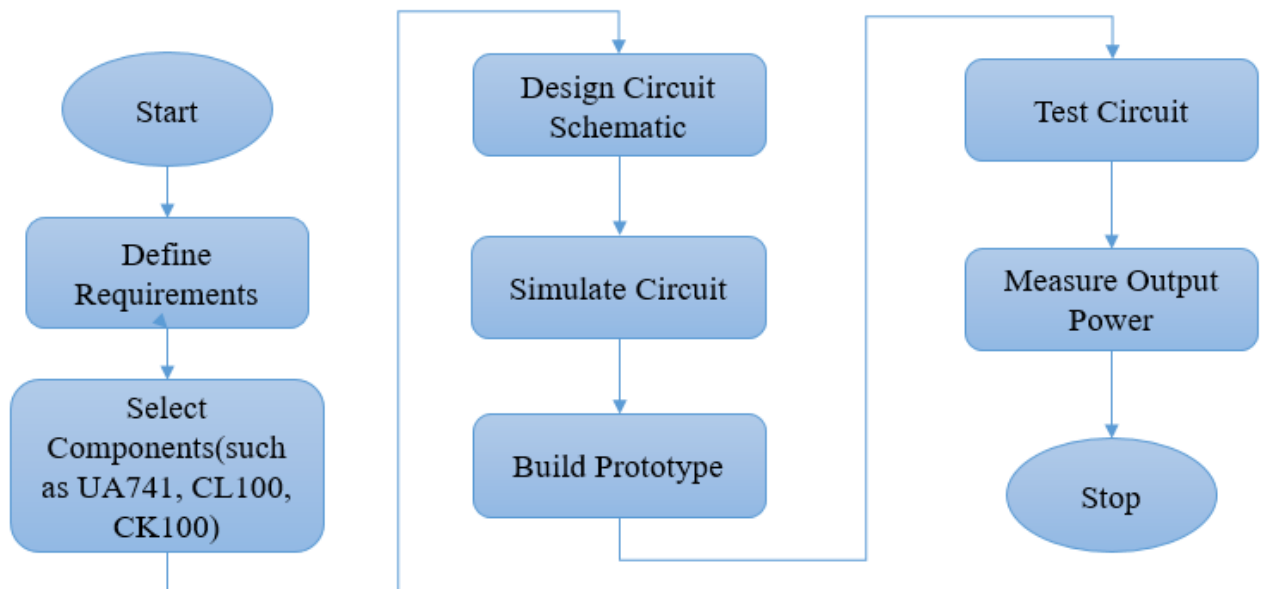

## 2.5 CIRCUIT DIAGRAM

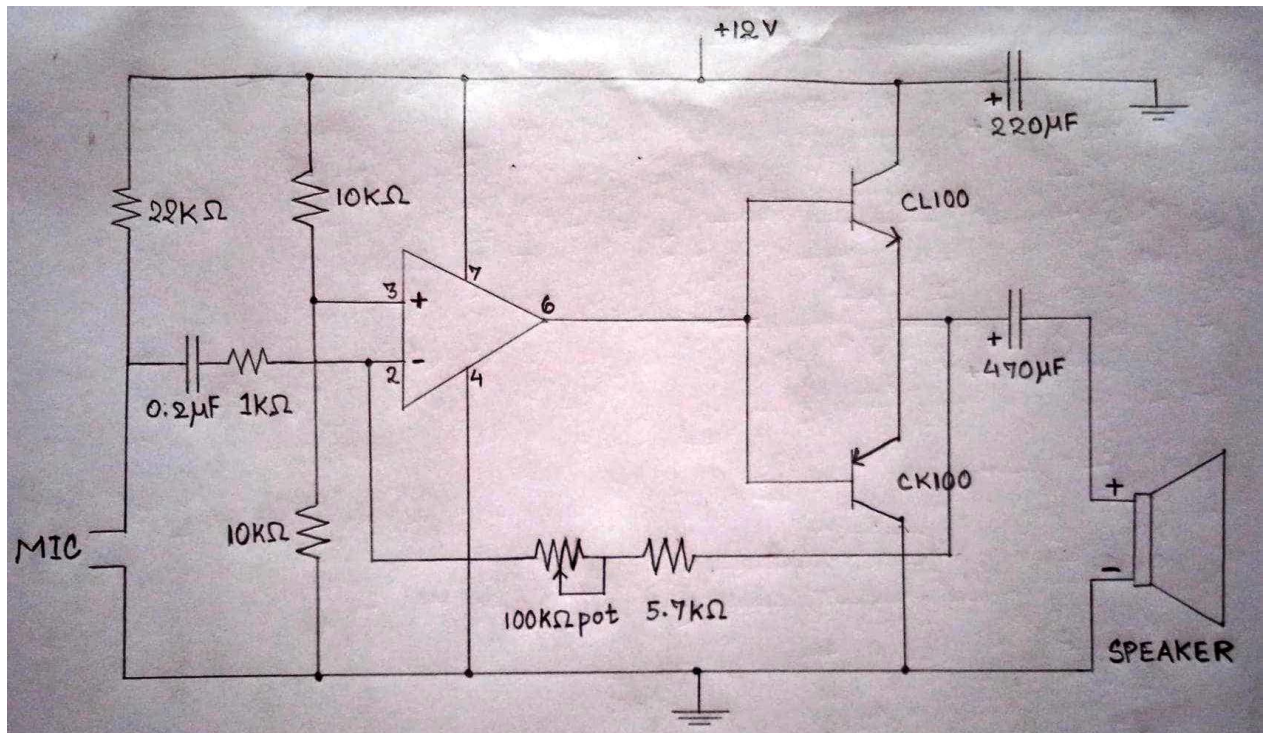

## 2.6 COMPONENT LIST

Component	Specification	Quantity
Operational Amplifier	UA741	1
Transistors	CL100	1
	CK100	1
Potentiometer	100K	1
Microphone	Electret Condenser Microphone	1
Speaker	4 Ω, 3 W	1
Resistors	1KΩ	1
	5.7KΩ (5.6KΩ + 100Ω)	1
	10KΩ	1
	22KΩ	1
Capacitors	0.2μF, Ceramic	1
	220μF, Electrolytic	1
	470μF, Electrolytic	1
Breadboard	-	1

## **2.7 DETAILED DESCRIPTION**

### **Working Principle:**

The audio amplifier circuit amplifies low-power audio signals to a higher power suitable for driving speakers. The UA741 operational amplifier is used for pre-amplification, while CL100 and CK100 transistors are used for power amplification. Below is a detailed description of the various components and their roles in the circuit:

#### **1. Microphone (MIC):**

- **Purpose:** Captures the audio signal.
- **Description:** The microphone converts sound waves into an electrical signal, which serves as the input to the amplifier circuit.

#### **2. Input Stage:**

- **Components:**

- 0.2 $\mu$ F Capacitor
- 1k $\Omega$  Resistor
- 10k $\Omega$  Resistor

- **Description:** The audio signal from the microphone passes through a 0.2 $\mu$ F coupling capacitor, which blocks any DC components. The signal then passes through a 1k $\Omega$  resistor, which works with the 10k $\Omega$  resistor to form a voltage divider, setting the appropriate input voltage level for the operational amplifier (op-amp).

#### **3. Operational Amplifier (UA741):**

- **Pins:**

- Pin 2: Inverting Input
- Pin 3: Non-Inverting Input
- Pin 4: Negative Power Supply
- Pin 6: Output
- Pin 7: Positive Power Supply

- **Description:** The UA741 is configured as a non-inverting amplifier. The audio signal is fed into the non-inverting input (pin 3). The feedback network consisting of a 100k $\Omega$  potentiometer and a 5.7k $\Omega$  resistor connected between the output (pin 6) and the inverting input (pin 2) sets the gain of the amplifier.

#### **4. Transistors (CL100 and CK100):**

- **Purpose:** Provide additional amplification and drive the speaker.

- **Description:**

- **CL100:** Acts as a current amplifier, receiving the output from the UA741 and boosting the current to drive the CK100 transistor.
- **CK100:** Further amplifies the current to provide sufficient power to the speaker.

- **Connections:**


- The collector of the CL100 is connected to the +12V power supply through a 220 $\mu$ F capacitor, which stabilizes the voltage supply.
- The emitter of the CL100 is connected to the base of the CK100, forming a Darlington pair configuration for higher current gain.
- The CK100's collector is connected to the speaker through a 470 $\mu$ F capacitor, which blocks DC and allows AC signals to pass, ensuring only the amplified audio signal reaches the speaker.

## 5. Output Stage:

- **Speaker Specifications:** 4 $\Omega$ , 3W
- **Description:** The amplified audio signal is fed into the speaker, converting the electrical signal back into sound.

This detailed description and analysis provide a comprehensive overview of the audio amplifier circuit, highlighting its design, component functions, and performance metrics.

## 2.8 RESULT AND ANALYSIS

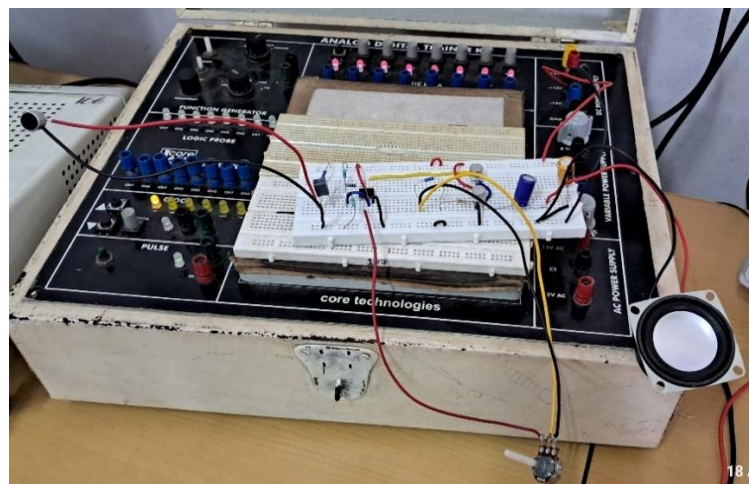

### Testing of the Circuit:

During the testing phase of our audio amplifier circuit, we provided an input signal with an amplitude of 150mV peak-to-peak. The output signal measured at the speaker terminals had an amplitude of 7V peak-to-peak.



To calculate the amplification factor (gain) of the circuit, we use the formula:

$$\text{Gain} = \frac{\text{Output Amplitude}}{\text{Input Amplitude}}$$

$$\text{Gain} = \frac{7V}{150mV} = 46.67$$

Thus, the amplification factor (gain) of the audio amplifier circuit is 46.67.

These results indicate that our audio amplifier circuit successfully amplified the input signal by a factor of 46.67, demonstrating effective performance in boosting the signal to drive the  $4\Omega$  speaker with adequate power.

#### Output Power Measurement:

- **Voltage Measured Across Speaker:**  $7V_{PP} = \frac{7}{2\sqrt{2}} V_{RMS} = 2.475 V_{RMS}$
- **Speaker Resistance:**  $4\Omega$
- **Calculated Power:**  $P = \frac{(V_{RMS})^2}{R} = \frac{(2.475 V_{RMS})^2}{4\Omega} = 1.531W$

This calculated power output confirms that the amplifier provides sufficient power to the  $4\Omega$  speaker while staying well within its 3W power rating. The analysis verifies that the amplifier design meets the intended specifications and operates effectively within safe parameters, ensuring the longevity and reliability of both the amplifier and the speaker.

**Output Sound Quality:** The sound quality was assessed subjectively by listening to the amplified output through the speaker. The audio output was clear and free from noticeable distortion, indicating that the amplifier preserved the integrity of the input signal while providing sufficient power.

## 2.9 CONCLUSION

The audio amplifier circuit designed in this project successfully amplified audio signals to a suitable level for driving a  $4\Omega$  speaker, showcasing a practical application of theoretical electronics concepts. By employing the UA741 operational amplifier along with CL100 and CK100 transistors, the project offered valuable insights into the selection, characteristics, and limitations of these components. The UA741 op-amp was pivotal in the pre-amplification stage, providing the necessary voltage gain, while the CL100 and CK100 transistors facilitated current amplification in the power stage, ensuring efficient signal enhancement with minimal distortion.

The hands-on experience in circuit design and implementation was a critical component of this project. Setting up the feedback network for the op-amp to determine the desired gain and designing the complementary push-pull stage using power transistors required meticulous attention and precise component arrangement. This process underscored the significance of practical skills in creating a functional and efficient amplifier circuit. Additionally, the iterative cycle of testing, troubleshooting, and refining the circuit highlighted the essential role of diagnostics in resolving issues and optimizing performance.

Several advantages were apparent in the chosen design. The circuit's high amplification factor (46.67) provided a substantial boost from the input signal of 150mV peak-to-peak to an output of 7V peak-to-peak. The use of widely available and cost-effective components like the UA741, CL100, and CK100 made the design economical and accessible. The adjustable gain feature, facilitated by the 100k $\Omega$  potentiometer, allowed for flexible tuning to meet specific requirements. Capacitive coupling effectively blocked DC components, ensuring that only the AC audio signal was amplified. The Darlington pair configuration of the transistors significantly improved the current driving capability, essential for delivering sufficient power to the speaker. Additionally, power supply decoupling capacitors contributed to stability and noise reduction, resulting in cleaner amplification.

Efficiency and performance optimization were key learning outcomes, particularly in understanding the trade-offs between different amplifier classes. The Class AB configuration of the power stage successfully balanced efficiency and distortion, making it suitable for real-world applications. Managing heat dissipation with appropriate heat sinks ensured the circuit's reliability and stability under various operating conditions.

This project also emphasized the importance of bridging theoretical knowledge with practical application. Concepts such as feedback, gain, frequency response, and signal amplification were not only understood but also applied in a hands-on environment, reinforcing theoretical learning with tangible results. This integration is crucial for developing a comprehensive understanding of electronics and for preparing for more complex projects in the future.

Overall, the project was a success, achieving a clear, powerful output suitable for driving a 4 $\Omega$  speaker with an output power of 1.531W. The amplifier circuit not only met the design goals but also provided a robust platform for future exploration and enhancement. Potential future work could involve investigating different amplifier classes, integrating digital signal processing (DSP) for enhanced audio control, or designing more complex multi-stage amplification systems for improved



performance. This project lays a solid foundation for these advancements, significantly contributing to ongoing learning and development in the field of electronics and communication engineering.

## 2.10 REFERENCES

1. Gupta, A., Sharma, P., & Verma, R. (2021). Research and Design of Suitable Power Amplifier for Application in The Area of Sound Selection and Enjoyment. *Journal of Audio Engineering*. [[https://www.researchgate.net/publication/348652615\\_Research\\_and\\_Design\\_The\\_Suitable\\_Power\\_Amplifier\\_for\\_Application\\_in\\_The\\_Area\\_of\\_Sound\\_Selection\\_and\\_Enjoyment](https://www.researchgate.net/publication/348652615_Research_and_Design_The_Suitable_Power_Amplifier_for_Application_in_The_Area_of_Sound_Selection_and_Enjoyment)]
2. Jones, T., & Smith, R. (2019). High-Fidelity Audio Amplifier Design. *Journal of Audio Engineering*. [<https://secure.aes.org/forum/pubs/journal/?elib=255>]
3. Brown, M., & Lee, C. (2018). Power Efficiency in Audio Amplifiers. *IEEE Transactions on Consumer Electronics*.
4. <https://www.alldatasheet.com/datasheet-pdf/pdf/25555/STMICROELECTRONICS/UA741.html>
5. <https://www.alldatasheet.com/datasheet-pdf/pdf/123595/CDIL/CL100.html>
6. <https://www.alldatasheet.com/datasheet-pdf/pdf/123600/CDIL/CK100.html>
7. <https://components101.com/misc/electret-condenser-microphone>
8. <https://www.youtube.com/watch?v=Mv6Z9PNUyhM>
9. <https://www.youtube.com/watch?v=aSXv6FdYQfM>